

HOW TO SOLVE YOUR ANTENNA MATCHING PROBLEMS

John Sexton, G4CNN.

Reprinted from Echelford Amateur Radio Society Newsletter for November 1978.

Introduction.

In January 1977 there appeared in RADCOM an article by G6XN extolling the virtues of the Smith Chart. Having recently acquired a programmable calculator with magnetic cards for permanently keeping programs I decided to have a go at discovering the underlying 'Maths' and writing programs to do the job.

I succeeded and now have a suite of programs on just 2 cards which will do all that a Smith chart will. I realise that Maths is not everybody's cup of tea, but it is really much easier to get the right answers this way. Trying to find the correct point on the chart is not very easy, especially as you get older and your eyes are not what they once were.


However the over-riding reason for doing it this way is that Smith charts are not easily available:

A Non-calculator method.

Let me allay your fears. I am not about to give the details of a computer program. It turned out that the calculations are not very difficult and if you can remember how to do squares and square-roots, this is enough.

So here we go.

Some Basics.

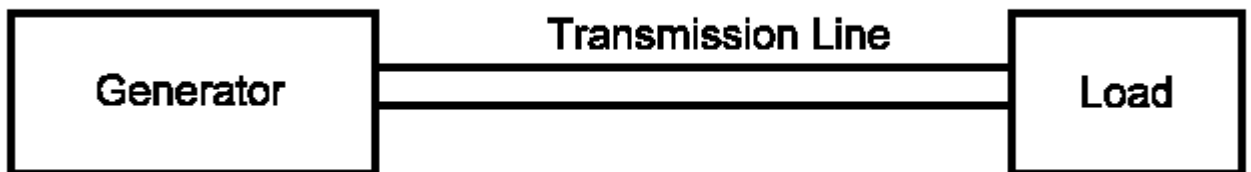

If the transmission line has an impedance Z_0 and if the load has an impedance Z_0 then the line is matched and the SWR is 1. However long the line is (assuming no losses) the generator (transmitter) will see a constant non-reactive resistance Z_0 . (e.g. 75 ohms).


But if the load is reactive, or not equal to the characteristic impedance of the line, then the line is not matched and will have standing waves on it. They have a pattern which repeats every half wavelength.

Provided that the line is not too lossy and that the transmitter can cope, the load will get as much power as in the matched case. If the load is an antenna it will radiate just as much power.

The reasons for keeping the SWR down are:-

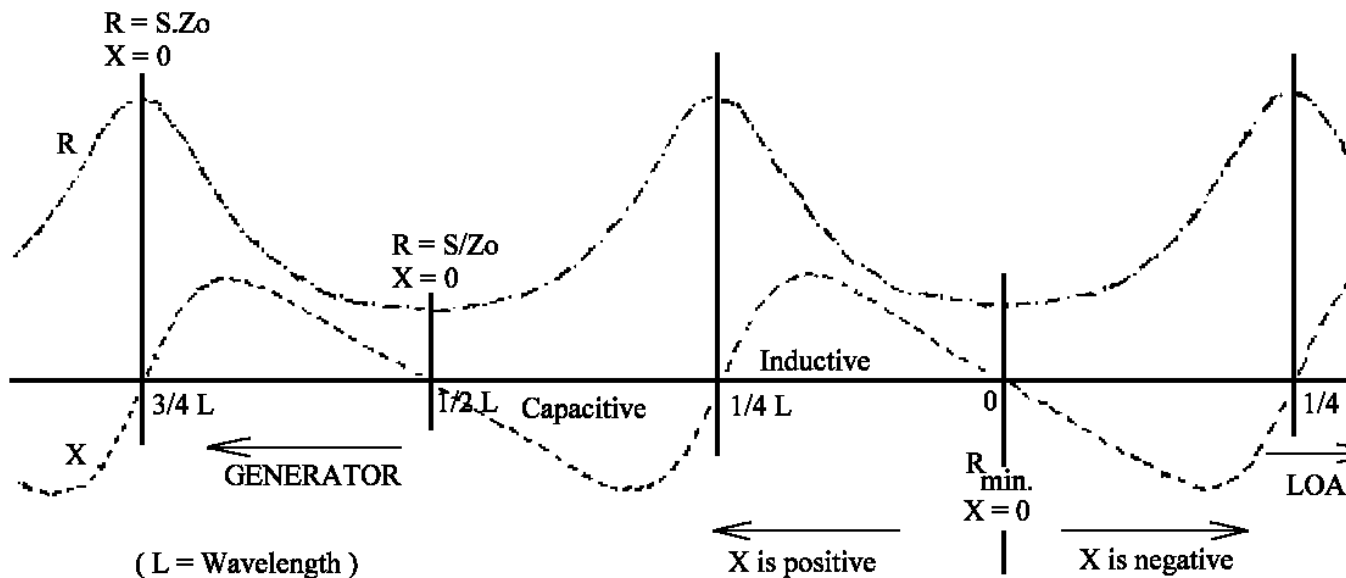1. High voltages and currents can be generated at points on the line causing insulation problems.
2. The transmitter probably can't cope with very much reactance nor a load which is too far from its nominal output impedance.
3. At high frequencies and high SWR'S, line losses can be significant.

$$\text{Wavelength in Feet} = \frac{299.79}{f} * 3.281 * \text{velocity factor}$$



The diagram shows the way in which the resistance R and the reactance X vary along the transmission line in a repeating pattern. Of course, allowance must be made for the velocity factor (0.66 - 0.8 for typical coaxial cables, semi-air spaced 0.8 - .95, open wire feeder 0.95 - 0.98), when working out the wavelength. Use the formula inset above, with f equal to the frequency in MHz.

IMPEDANCE and SWR

The SWR is constant all along the line but the impedance varies from point to point. The impedance at a particular point has a resistive part R and a reactive part X. The values of R and X are fixed by the SWR and the distance from any point of minimum resistance, which is used as a convenient zero point.

FOUR NUMBERS.

R for resistance.

X for reactance.

S for SWR

E for distance in electrical degrees. ($90^\circ = 1/4$ of a wavelength) from a point of minimum resistance. (positive degrees towards the transmitter).

These four quantities are connected with one another. If you know any two of them, you can find the other two. For example, if you know R and X, then you can find S and E, or conversely given S and E you can find R and X.

This is what the Smith Chart does for you.

DOING WITHOUT THE 'SMITH' CHART

Here are the formulae which allow you to calculate R,X,S or E.

Important

r stands for R/Zo

x stands for X/Zo

t stands for TAN(E)

There are 6 CASES depending on what you know and what you what to find out.

CASE 1. R and X known.

$$S = \frac{1 + r^2 + x^2}{2r} + \sqrt{\left(\frac{1 + r^2 + x^2}{2r}\right)^2 - 1}$$

$$t = \frac{rS - 1}{x}$$

and

CASE 2. S and E known.

Important S must be greater than 1.

$$r = \frac{S(1 + t^2)}{S^2 + t^2}$$

$$x = \left(1 - \frac{r}{S}\right)t$$

and

CASE 3. R and S known.

Important., To get a solution $S \geq r \geq 1$ or $1/S \leq r \leq 1$

$$x = \pm \sqrt{(rS - 1) \left(1 - \frac{r}{S}\right)}$$

$$t = \frac{rS - 1}{x}$$

Actually there are two possibilities. Either both x and t are positive or they are both negative.

CASE 4. X and E known.

Important. To get a solution in this case, t must be greater than or equal to x, in numerical value, i.e. ignoring +/- signs.

$$S = \sqrt{\frac{t(1+tx)}{t-x}}$$

$$r = \frac{1+tx}{S}$$

CASE 5. S and X known.

$$r = \frac{1}{2} \left(S + \frac{1}{S} \right) \pm \sqrt{\frac{1}{4} \left(S + \frac{1}{S} \right)^2 - 1 - x^2}$$

$$t = \frac{Sr - 1}{x}$$

If the quantity under the square-root is negative then there is no solution. Either S is wrong or X is wrong. The \pm sign means that there are two possible solutions.

CASE 6. R and E known.

$$S = \frac{1+t^2}{2r} \pm \sqrt{\left(\frac{1+t^2}{2r}\right)^2 - t^2}$$

$$x = \left(1 - \frac{r}{S}\right)t$$

If $R < Z_0$ then take the positive signs only.

If $R \geq Z_0$ then both + and - signs give solutions.

X always has the same sign as t.

SOME LIMITATIONS.

If you try to use these formulae with made up values that don't correspond to reality, you may run into difficulties. For example you may find you have to take the square-root of a negative number.

If this happens, nothing can be done. Your starting values are impossible. Unfortunately even for some legitimate values you can also run into problems. This will appear as an attempt to divide by zero. This can be avoided if you first check to see if you are dealing with one of five special cases which are specially easy to solve. These cases are:

	R	x	S	E	Answer
1.	$> Z_0$	$= 0$	$= r$	$= 90^\circ$	High resistance, High voltage point
2.	$< Z_0$	$= 0$	$\frac{1}{r}$ $= r$	$= 0^\circ$	Low resistance, High current point
3.	$= Z_0$	$= 0$	$= 1$		A matched line, no point of minimum resistance and hence no value for E
4.	$= ?$	any value	$= ?$	$= 90^\circ$	In this situation X cannot be measured. It seems to take all values at once. At all other points, $R=0$ and $X=Z_0.\tan(E)$
5.	$= 0$	$Z_0.\tan(E)$	$= ?$	Any (not 90°)	

HOW TO USE THE FORMULAE

First check to see if you are dealing with one of the 5 special cases. If so then the values of the unknowns are as given above. If not then decide which of the four parameters you know and choose the appropriate formula for the other two.

Example.

1) A short vertical is tuned to resonance but the SWR measured at the Tx is still 4:1. What is the impedance of the antenna? The antenna is fed with 50 ohm co-ax. Since the antenna is resonant, the reactance $X = 0$. Therefore this is one of the special cases. Short verticals have a low resistance so this must be special case 2, where R,

$$Z_0, X = 0, \quad S = \frac{1}{r} \text{ and } E = 0.$$

$$\text{Therefore } r = \frac{1}{S} = \frac{1}{4}. \text{ Remember that } r = R/Z_0$$

$$\text{Therefore } R = \frac{1}{4} Z_0 = 12 \frac{1}{2} \text{ ohms.}$$

Example 2.

Because of the lack of space a dipole put up for 40 metres is too short. It is only 58 feet long. It is centre fed with 75 ohm twin which has, a length of 44 feet. It is found to be impossible to match because of the high impedance and a check on the SWR shows it to be around 7.5. What can be done?

Well there are a number of possible solutions, but first of all it helps to know whats going on.. A check with a Neon suggests that the shack end of the feeder is at a voltage maximum, so $E = 90^\circ$ here. The velocity factor of the cable is about 0.71 so one wavelength is about 99 feet 9 inches.

So a 44 foot feeder represents 158.75 electrical degrees.

So at the antenna. $E = 90^\circ - 158.75^\circ = -68.75^\circ$ Remember that distances measured towards the Tx are positive, so towards the antenna the distance is considered negative.

Thus we have., $S=7.5$ $E= -68.75^\circ$ and we can try to find R and X at the antenna.

This is general case number 2.

$$\text{Therefore } r = \frac{7.5 \cdot (1 + (\tan(-68.75))^2)}{7.5^2 + (\tan(-68.75))^2} = 0.9082$$

$$\text{and } x = \left(1 - \frac{0.9082}{7.5}\right) \cdot \tan(-68.75) = -2.26$$

Remember that $R = r \cdot Z_0$ and $X = x \cdot Z_0$

Therefore $R = 0.9082 \times 75 = 68$ ohms approx

and $X = -2.26 \times 75 = -169.5$ ohms approx

Obviously the problem is the high reactance, and, being negative and hence capacitive, can be compensated for by coils at the antenna, one in each leg of the feeder.

For their values $\omega L = 169.5 / 2 = 84.75$ ohms

Therefore the inductance L needs to be = 1.9 microhenries.

----- 000000 -----

SOME OTHER USEFUL FORMULAE.

When dealing with an antenna wire we are dealing with the special case where $R = ?$ $S = ?$ and $E = 90^\circ$ at the outer end. The reactance at any point, can be calculated from the formula:

$$X = Z_0 \cdot \tan(E)$$

To estimate Z_0 use

$$Z_0 = 276 \log\left(\frac{\lambda}{d}\right) - 120 \text{ ohms} \quad \text{for a dipole}$$

$$\text{or } Z_0 = 138 \log\left(\frac{\lambda}{d}\right) - 104 \text{ ohms} \quad \text{for a single end-fed wire.}$$

----- 000000 -----

LINE LOSSES.

When line losses are significant, SWR varies along the line, being greatest at the load end.

If S_1 , S_2 are the SWRs at the generator and load ends of the line and L = the total matched line loss in dBs then,

to calculate S_1 from S_2 :

$$\text{Calculate: } V_2 = \frac{S_2 - 1}{S_2 + 1} \quad \text{and} \quad V_1 = 10^{-L/10} V_2$$

$$\text{Then } S_1 = \frac{1 + V_1}{1 - V_1}$$

To do it the other way round, just reverse the calculation procedure.